 


Physical hardware and setup

Hardware requirements, exact jumper map, firmware setup, bring-up, and safety guidance


SmartDoor uses a computer webcam as the QR scanner. The ESP32 is only the door actuator: it connects to Wi-Fi and MQTT, receives an authorized unlock command, activates a relay that powers the solenoid, operates the indicators, and relocks automatically.



SmartDoor ESP32, high-active relay, and 12 V solenoid wiring diagram

All ground symbols on the logic side connect to ESP32 GND. The separate lock-supply negative connects only to the solenoid circuit; the relay contacts provide the switching isolation.

Additional component-layout reference

 


Conceptual SmartDoor component-layout reference

Reference only: this supplied image depicts a generic relay module and still shows a 5 V/12 V lock choice. For the actual build, use the verified diagram above: the lock supply is **12 V**, the pictured relay input is **IN1**, and the physical **COM/NO** screw terminals must be identified with a continuity meter.

On the pictured relay module, the diagram's IN terminal is printed as IN1. Leave the blue jumper installed across VCC and JD_VCC for the single-supply setup documented here.

SMARTDOOR — YOUR ESP32 PIN LOCATIONS

 30-pin ESP32 DevKit V1-compatible board • USB-C at the bottom



ESP-32
Wi-Fi • Bluetooth

CONNECT THESE SIX PINS

- VIN** → relay VCC
5 V logic power
- GND** → relay GND
Also connect the LED and piezo ground rail
- D18** → relay IN1
HIGH = unlock
- D19** → 220–330 Ω resistor
Then connect the red LOCKED LED
- D21** → 220–330 Ω resistor
Then connect the green UNLOCKED LED
- D5** → passive piezo positive (+)

IMPORTANT
The pictured board has bare side holes.
Solder two 1×15 headers before using jumpers.

USB-C

Use the printed labels on the physical board as the final check before applying power.

Exact SmartDoor pins on the pictured 30-pin USB-C ESP32 board

1. Hardware requirements

Required for the supported prototype

Quantity	Part	Requirement or example
1	Computer	Runs Docker, the SmartDoor web application, Mosquitto, and the webcam scanner
1	Webcam	Built-in or USB camera capable of reading the displayed QR code
1	Wi-Fi network	2.4 GHz network reachable by both the computer and ESP32; client isolation must be disabled
1	ESP32 development board	The pictured 30-pin ESP32 DevKit V1-compatible USB-C board
1	USB-C data cable	Must support data as well as power; charge-only cables cannot upload firmware
2	1x15, 2.54 mm male pin headers	Solder to the pictured board if its side headers are not already installed
1	CE Store solenoid door lock	Confirmed 12 V, power-on-to-unlock model
1	Regulated 12 V DC lock supply	Current rating must cover the lock's inrush and continuous current with margin
1	Pictured 1-channel relay module	5 V SRD-05VDC-SL-C relay board labeled VCC, IN1, GND, and VCC/JD_VCC
1	Regulated 5 V logic supply	Powers only the relay module if the ESP32 board's USB 5V/VIN pin is not used
1	Flyback diode	Reverse-voltage and forward-current ratings must exceed the lock supply voltage and measured coil current
1	Inline fuse and holder	Size from the seller-confirmed/measured normal and inrush current and the wire rating
1 each	Red and green LED	Standard low-current 3 mm or 5 mm LED
2	220-330 ohm resistor	One current-limiting resistor for each LED
1	Passive piezo buzzer	A small, high-impedance piezo suitable for an MCU signal; do not attach a speaker or high-current siren directly
1 each	Terminal block, enclosure, and hookup wire	Wire, connectors, and fuse must be rated for the measured lock current
1 each	Breadboard and jumper-wire set	Use the breadboard only for ESP32 logic; use secure terminals for the solenoid-current path

The ESP32 can be powered from its USB cable. The relay module needs 5 V and must share logic ground with the ESP32. The solenoid uses its separate regulated 12 V DC supply through the isolated relay contacts; never connect 12 V to an ESP32 or relay-logic pin.

Software requirements

- Docker Desktop with Docker Compose
- VS Code with the PlatformIO IDE extension, or PlatformIO Core (pio)
- A modern browser with camera permission enabled for `http://localhost:5173`
- USB serial driver for the development board when the operating system does not install one automatically (commonly CP210x or CH340)

Relay requirements and 3.3 V input check

The pictured module uses an SRD-05VDC-SL-C 5 V relay. Read the contact ratings printed on the actual relay case and verify that the solenoid's measured inrush and steady current are safely below its DC rating. An AC contact rating must not be treated as an equal DC rating.

The blue jumper in the photo bridges VCC and JD_VCC, allowing one 5 V logic supply to power both the module input circuit and relay coil. Keep it installed for this setup. Removing it requires a separately designed relay-coil supply and is not needed here.

The module is powered at 5 V, but an ESP32 outputs only 3.3 V on GPIO 18. Before connecting the lock, power the module at 5 V and verify that `IN1 = LOW` leaves the relay off and `IN1 = 3.3 V` makes it click. This confirms both 3.3 V compatibility and high-active behavior. If it does not switch reliably, add a non-inverting 3.3-to-5 V logic buffer such as a 74AHCT125 with a 10 kohm pull-down on its input. Never apply 5 V to an ESP32 GPIO.

Do not infer NC, COM, and NO from the screw terminal's vertical position when the printing is unclear. Identify them with a continuity meter while the lock supply is disconnected:

1. With the relay off, find the two connected terminals; they are COM and NC. The remaining terminal is NO.
2. Energize the relay input and find the new connected pair; they are COM and NO.
3. The terminal present in both connected pairs is COM. Label all three terminals before adding lock wiring.

2. Jumper and wiring instructions

Disconnect USB and the 12 V lock supply while assembling the circuit.

For the pictured board, hold it with the ESP32 antenna at the top and USB-C connector at the bottom. VIN and GND are the bottom two pins on the left header. The four firmware GPIO pins are consecutive on the middle of the right header in this order from top to bottom: D21, D19, D18, D5. Use the printed labels on the actual board as the final check before powering it.

ESP32 connection	Connect to	Notes
ESP32 GPIO 18 (D18)	Relay module IN1	High-active unlock signal; first verify that the module recognizes 3.3 V
ESP32 5V/VIN while USB-powered	Relay module VCC	Relay module requires 5 V; do not use ESP32 3V3
ESP32 GND	Relay module GND	Logic-side common ground is required
12 V supply positive	Inline fuse, then relay COM	This is the separate lock-power circuit, not relay logic power
Relay NO	Solenoid red wire	NO closes to COM only during an unlock; leave NC unused
Solenoid black wire	Lock-supply negative	Observe the product's red-positive, black-negative polarity
Flyback diode cathode (striped end)	Solenoid red / relay-NO node	Reverse-biased during normal operation
Flyback diode anode (unstriped end)	Solenoid black / supply-negative node	Never reverse these diode connections
GPIO 19 (D19)	220-330 ohm resistor, then red LED anode (long leg)	Red means locked
ESP32 GND	Red LED cathode (short leg/flat side)	The resistor may be placed on either side of the LED
GPIO 21 (D21)	220-330 ohm resistor, then green LED anode (long leg)	Green means unlocked
ESP32 GND	Green LED cathode (short leg/flat side)	Do not omit the resistor on physical hardware
GPIO 5 (D5)	Passive piezo +	Firmware produces a 1600 Hz, 120 ms tone
ESP32 GND	Passive piezo -	Use a transistor driver for an active buzzer or any device exceeding the GPIO rating

The resulting connections are:

```

ESP32 5V/VIN ----- relay VCC
ESP32 GND ----- relay GND
ESP32 D18 ----- relay IN1 (HIGH = unlock)

12 V supply + ---- fuse ---- relay COM
relay NO ----+---- red [ 12 V SOLENOID ] black ---- 12 V supply -
| flyback |
+-----|<|-----+
stripe toward red
relay NC ---- not connected

ESP32 D19 ---- 220-330 ohm ----|>|-- GND red LED
ESP32 D21 ---- 220-330 ohm ----|>|-- GND green LED
ESP32 D5 -----( )-- GND passive piezo

```

The flyback diode's striped cathode connects to the red/positive side and its unstriped anode connects to the black/negative side. It must not conduct while the solenoid is energized; it conducts only when the relay opens and clamps the inductive voltage spike. The diode already visible on the relay board protects the small relay coil, not the external door-lock solenoid.

At startup GPIO 18 stays low, the high-active relay remains off, COM remains disconnected from NO, and the solenoid stays de-energized. An accepted command drives GPIO 18/IN1 high, closes COM to NO, energizes the solenoid, changes the indicator to green, sounds the piezo, and drives GPIO 18 low again after five seconds. The firmware also switches the relay off if Wi-Fi or MQTT connectivity is lost.

3. Host application setup

From the repository root:

```
cp .env.example .env
docker compose up --build -d
docker compose stop device-simulator
docker compose ps
```

Edit `.env` before exposing the system beyond a private development network. At minimum, replace `SMARTDOOR_ADMIN_PASSWORD`, `SMARTDOOR_QR_SECRET`, and `MQTT_PASSWORD`. Stopping `device-simulator` is important because the simulated and physical actuators subscribe to the same command topic and would otherwise unlock together.

Find the computer's private LAN address, such as `192.168.1.25`. The ESP32 must use this address for `MQTT_HOST`; `localhost` means the ESP32 itself, `mosquitto` only resolves inside Docker, and `host.wokwi.internal` is only for Wokwi.

Confirm that the computer firewall permits inbound TCP port 1883 from the trusted local network. Do not expose this development MQTT listener to the internet; it does not use TLS.

4. ESP32 firmware setup

Create the local secrets file:

```
cp firmware/include/secrets.example.h firmware/include/secrets.h
```

Edit `firmware/include/secrets.h` for the physical network:

```
#pragma once
#define WIFI_SSID "YOUR_2_4_GHZ_WIFI_NAME"
#define WIFI_PASSWORD "YOUR_WIFI_PASSWORD"
#define MQTT_HOST "192.168.1.25"
#define MQTT_PORT 1883
#define MQTT_USERNAME "smartdoor"
#define MQTT_PASSWORD "THE_VALUE_FROM_DOT_ENV"
#define SMARTDOOR_RELAY_MODE 1
```

`secrets.h` is excluded from Git. The Wi-Fi network must provide internet access to `pool.ntp.org`, because the firmware rejects MQTT commands when its clock is not synchronized.

Connect the ESP32 by USB, then build and upload from the repository root:

```
cd firmware
pio run
pio run --target upload
pio device monitor
```

If PlatformIO cannot choose the correct serial port, list available ports with `pio device list`, then run the upload with `--upload-port`, for example:

```
pio run --target upload --upload-port /dev/cu.usbserial-0001
```

The serial monitor speed is 115200 baud. The current firmware waits silently while connecting, so a device that never appears online usually has an incorrect Wi-Fi network, broker address, MQTT credential, blocked port, or unavailable NTP

connection. Press the ESP32 EN/reset button after correcting and reflashing it.

5. Bring-up and functional test

1. Double-check every connection with all power removed, especially the common ground and LED polarity.
2. Keep the VCC/JD_VCC jumper installed. With the solenoid and lock supply disconnected, power the relay module and test its 3.3 V IN1 response. Identify the screw terminals with a continuity meter, then confirm COM-NO is open at boot, closes only while GPIO 18 is high, and opens again after five seconds.
3. Remove all power, connect the fused solenoid circuit, then power the ESP32 and the regulated 12 V lock supply.
4. Open `http://localhost:5173`, sign in, and open **Door Status**.
5. Wait up to 20 seconds for ESP32-D00R-01 to show LOCKED and online. A heartbeat is sent every five seconds.
6. Create a user, grant **Main Door** permission, and add a schedule that includes the current time.
7. Issue a QR credential. Open **Webcam Scanner** and scan it, or upload the QR PNG.
8. Confirm this sequence: red LED off, green LED on, short tone, bolt retracts, then power is removed from the lock and the bolt extends after five seconds.
9. Open **Access Logs** and confirm the request progresses from GRANTED_COMMAND_SENT to UNLOCKED.

Test the electronics and software on the bench before mounting the lock. Then test repeatedly with the door open so a wiring, alignment, or software fault cannot lock anyone in or out. Keep the default five-second unlock time unless the seller confirms a longer coil duty cycle is safe.

6. Troubleshooting

Symptom	Checks
ESP32 never appears online	Use the computer's LAN IP for MQTT_HOST; check 2.4 GHz Wi-Fi, MQTT credentials, TCP 1883, Mosquitto health, and NTP access
SIM-D00R-01 responds instead	Run <code>docker compose stop device-simulator</code> ; only one actuator should serve D00R-01
ESP32 resets when the lock activates	Keep lock current off the ESP32 rails, verify the external flyback diode, shorten high-current wiring, and check supply voltage drop
Solenoid becomes hot	Remove power; verify that the supply is regulated 12 V, then confirm maximum energization time and duty cycle with the seller
LEDs do not light	Check polarity, series resistors, GPIO 19/21 placement, and the common ground
Relay does not click with GPIO high	Confirm the VCC/JD_VCC jumper is installed, relay VCC is 5 V, and grounds are common; measure GPIO 18/IN1; if 3.3 V is insufficient, add a non-inverting 3.3-to-5 V buffer
Access granted but no movement	Confirm relay mode is 1, use a meter to check COM-NO, verify red/black polarity and lock-supply voltage under load, and inspect the access log for device errors
MQTT authentication fails	Make <code>.env</code> and <code>secrets.h</code> credentials identical, rebuild and reflash, then restart the ESP32

7. Safety limits

This is an academic prototype. Do not install it on an emergency exit, fire door, or any opening where failure could endanger or trap a person. Do not rely on it as the sole access or life-safety mechanism. Keep low-voltage logic isolated from mains and lock power, fuse real-lock circuits appropriately, and provide a mechanical/manual release that works during power, network, and controller failures.